

Since the secondary is wound closely over central portion of primary, the same flux is also linked with turns of the secondary.

∴ Total magnetic flux through the secondary

$$N_s \Phi_B = \mu_0 N_s i A$$


By definition of the mutual inductance of the two coils is

Given by $M = \frac{N_s \Phi_B}{i} = \mu_0 N_p N_s A$

Measurement of Mutual Inductance →

The circuit diagram for measurement of mutual-inductance is shown in figure.

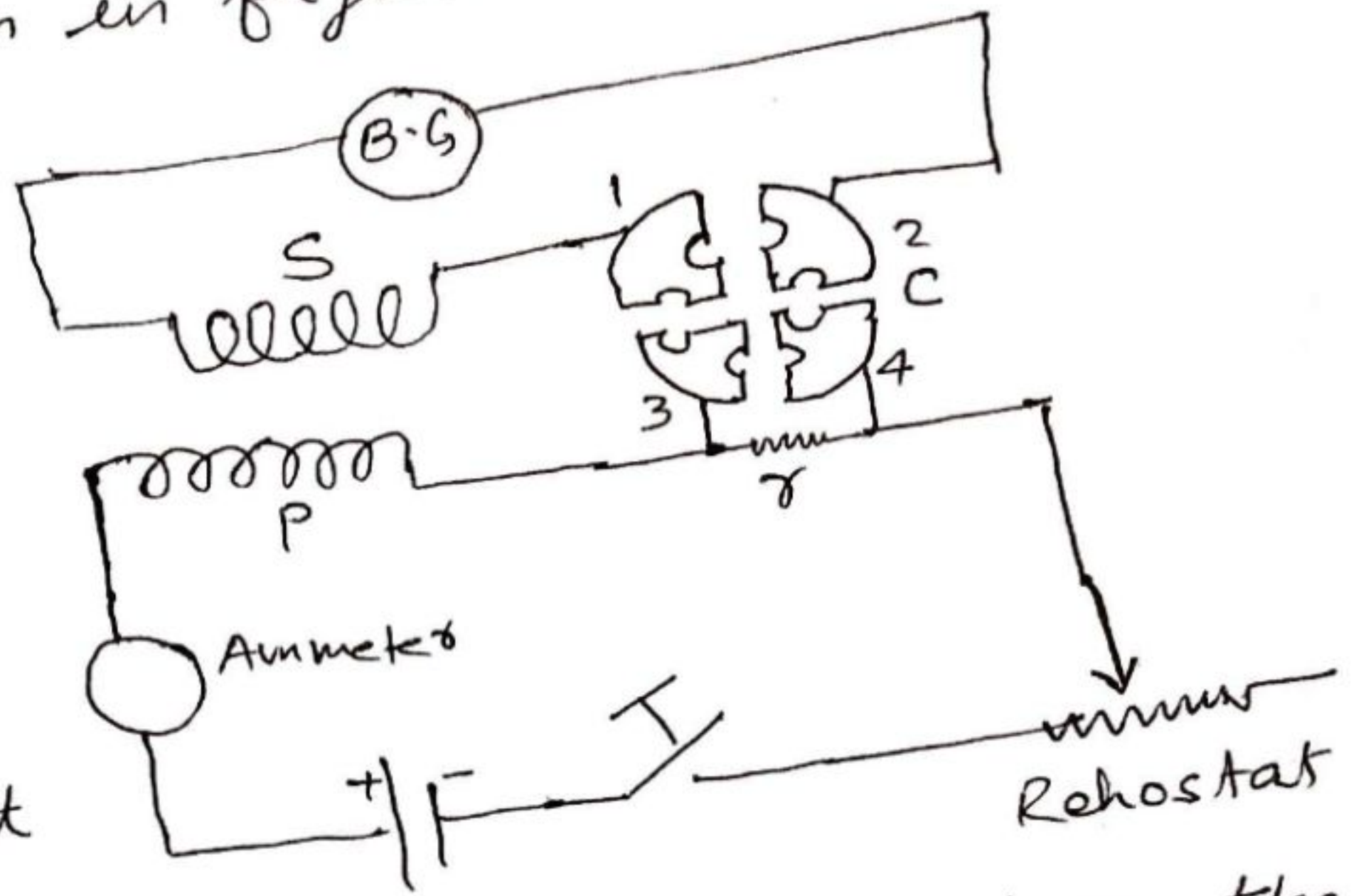Primary P and Secondary S are two coils whose mutual-inductance M is to be determined. Ballistic galvanometer (B.G) is C, is a four-segment commutator and 'r' is a very small resistance of the order of $\frac{1}{100} \Omega$



Workings → First of all, the segment

① and ② are connected together so that the Ballistic galvanometer and the secondary coil S form the closed circuit. The resistance r is kept short-circuited by connecting ③ and ④. The rheostat is adjusted so that a suitable current pass through the primary on depressing the key K. As key K is depressed the current in the primary P takes some time to grow and the flux through the secondary S changes during this time.

Hence an induced e.m.f is set up in the secondary and a momentary current flow and the galvanometer gives a deflection.

Let 'i' be the current at any instant in primary, the e.m.f induced in the secondary is given by

$$E = -M \frac{di}{dt}$$

The instantaneous current 'i' in the secondary is

$$i = \frac{E}{R} = \frac{-M}{R} \frac{di}{dt}$$

R = Total resistance of secondary circuit

Therefore, the charge dq passing through the galvanometer in a short time interval dt is given by

$$q = \int_0^{i_0} \frac{M}{R} di = \frac{M}{R} i_0$$

Let 'A' be the first observed throw of the coil of the

$$\theta = \frac{T}{2\pi} \cdot \frac{c}{NBA} \theta_1 \left(1 + \frac{\lambda}{2}\right) \quad \text{--- (3)}$$

where the symbols have their usual meanings

$$\text{Hence, } \frac{M}{R} i_0 = \frac{T}{2\pi} \frac{c}{NBA} \theta_1 \left(1 + \frac{\lambda}{2}\right) \quad \text{--- (1)}$$

To eliminate i_0 and $\frac{c}{NBA}$, the contacts between 1 and 2 and that between 3 and 4 are broken. The contact between 1 and 3 and that between 2 and 4 are made. The resistance r is now included in the primary circuit. The same steady current i_0 is now pass in the primary circuit. As the value of ' r ' is very small the steady current i_0 in the primary circuit remain unchanged. The potential difference across r is $i_0 r$ and it sends a steady current $\frac{i_0 r}{R}$ through the galvanometer.

Let ϕ be the steady deflection corresponding to this current then. --- (2)

$$\frac{i_0 r}{R} = \frac{c}{NBA} \phi$$

Dividing eqⁿ (1) by eqⁿ (2), we get

$$\therefore M = \frac{rT}{2\pi} \cdot \frac{\theta}{\phi} \left(1 + \frac{\lambda}{2}\right)$$